



Roll No.

JSS MAHAVIDYAPEETHA

JSS ACADEMY OF TECHNICAL EDUCATION, NOIDA

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

CIA-1 (AY 2024-25: Odd Semester)

Course : B. Tech
Semester : III
Subject : Network Analysis and Synthesis
Time : 1 hrs=60 min

Date : Oct 2024
Subject Code : BEC-303
Max. Marks : 20


COURSE OUTCOMES

C203.1	Understand basics of electrical circuits with nodal and mesh analysis.
C203.2	Apply electrical network theorems.
C203.3	Apply Laplace transform for analysis steady state and transient behaviour of network circuit
C203.4	Determine different network functions of Two Port network
C203.5	Analyse the frequency response of various filters.

SECTION-A

Attempt all the questions of this section



(1 X 5 = 5)

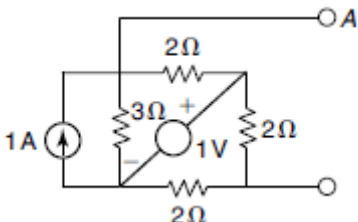Q. No.	Question	Marks	CO	BL/ KC*
1.	a How can an ideal voltage sources be converted into ideal current sources and vice-versa?	1	CO1	L2
	b Define the concept of Super-Mesh.	1	CO1	L1
	c List different types of dependent sources with its symbolic diagram.	1	CO1	L1
	d Define Reciprocity theorem.	1	CO2	L1
	e Find Thevenin impedance across the terminals AB of the given network 	1	CO2	L2

Section-B

Attempt all the questions of this Section

(3X3=9)

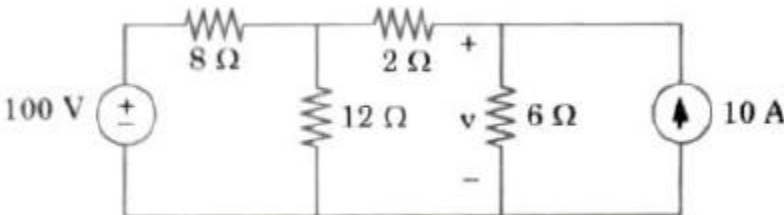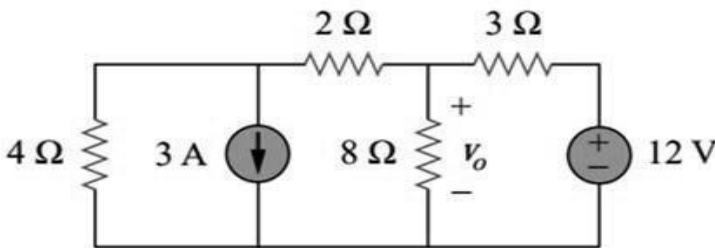2.	For the circuit shown in Fig., determine the voltage “v” using nodal analysis. 	3	CO1	L2
	OR Use source transformation to solve v_o in the following circuit: 			
3.	Find the Thevenin's equivalent circuit across the terminals a-b:	3	CO2	L3








Roll No.

JSS MAHAVIDYAPEETHA

JSS ACADEMY OF TECHNICAL EDUCATION, NOIDA

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

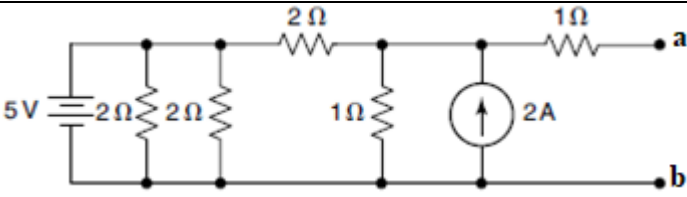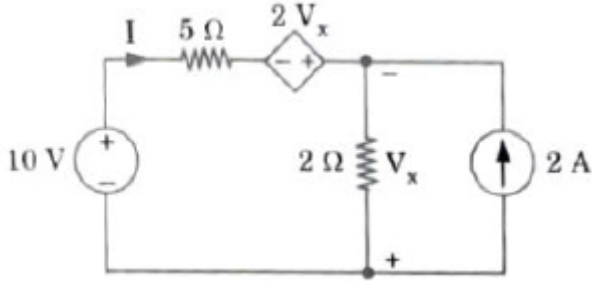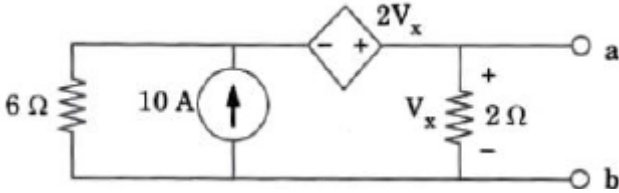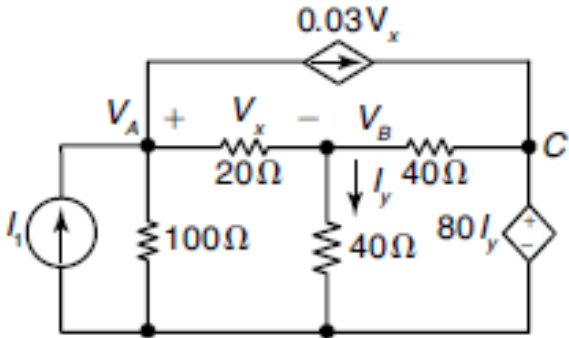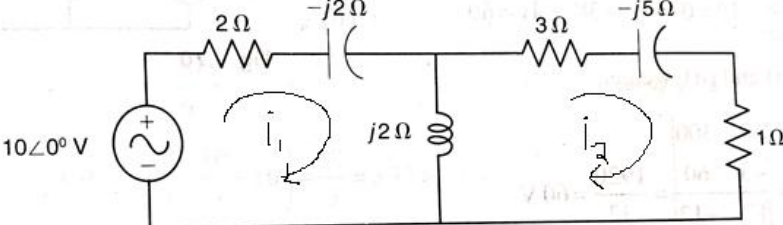	 <p>OR</p> <p>Show that the Thevenin's and Norton's Theorems are dual to each other with require circuits and equations.</p>			
4.	<p>Calculate the current I shown in Fig. by using superposition theorem.</p>  <p>OR</p> <p>Find the Norton equivalent circuit of the circuit in Fig. at terminals a-b</p> 	3	CO2	L3
Section-C				
Attempt all the questions of this Section (6X1=6)				
5.	<p>Use nodal analysis to find the voltages V_A, V_B and V_x in the circuit of Fig, in which $I_1=0.4$ A.</p>  <p>OR</p> <p>Find the loop current i_1 and i_2 in the figure given below.</p> 	6	CO1	L3



Roll No.										
----------	--	--	--	--	--	--	--	--	--	--

JSS MAHAVIDYAPEETHA

JSS ACADEMY OF TECHNICAL EDUCATION, NOIDA

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Dr. Deependra Sharma
(Faculty-EC1)

Dr. Shiva Ji Sinha
(Faculty-EC2)

Dr. Chandra Shankar
(Faculty-EC3)

Dr. Deependra Sharma
(Module Coordinator)

Dr. Chaya Grover
(NBA Coordinator)

Dr. Arun Kumar G
(HOD-ECE)